

# TECH TIP 60601

## Basic Temperature Measurements using IOtech DAQ Hardware

### INTRODUCTION

The most common devices used for sensing temperature include thermocouples, resistance temperature detectors (RTDs), and thermistors. Each has unique characteristics and properties that make one more suitable than another for a certain application.

*Thermocouples* are the most widely used device for sensing temperature, and probably the least understood. They are simple and efficient, and provide a small voltage signal proportional to the temperature difference between two junctions in a closed thermoelectric circuit. In its most basic configuration, one junction is held at a constant reference temperature while the other is placed in contact with the medium to be measured. This medium can be gas, liquid, or solid, but in all cases, the medium shall not be allowed to chemically, electrically, or physically contaminate or alter the thermocouple junction. For special applications or to protect them from the environment, thermocouples are available with protective coatings and shields or sheaths.

*RTDs* are composed of metals with a high positive temperature coefficient of resistance. Most RTDs are simply wire-wound or thin-film resistors made of wire with a known resistance vs. temperature relationship. Platinum is one of the most widely used materials for RTDs. They come in a broad range of accuracies, and the most accurate are also used as NIST (National Institute of Standards and Technology) temperature standards.

*Thermistors* are similar to RTDs in that they also change resistance between their terminals with a change in temperature. However, they can be made with either a positive or negative temperature coefficient. In addition, they have a much higher ratio of resistance change per degree C (several %) than RTDs, which makes them more sensitive.


### DISCUSSION

#### PART A — THERMOCOUPLES

##### *The Gradient Nature of Thermocouples*

Thermocouple junctions alone do not generate voltages. The output or potential difference that develops at the open end is a function of both the closed T1 junction and the T1' open end temperatures as shown in Figure 1. The principle of operation depends on the unique value of thermal emf generated between the open ends of the leads and the junction of two dissimilar metals held at a specific temperature. The principle is called the Seebeck Effect, named after the discoverer. The amount of voltage generated at the open ends of the sensor and the range of temperatures the device can measure depend on the Seebeck coefficient, which in turn depends upon the chemical composition of the materials comprising the thermocouple wire.

**Figure 1: Type T Basic Thermocouple Circuit**

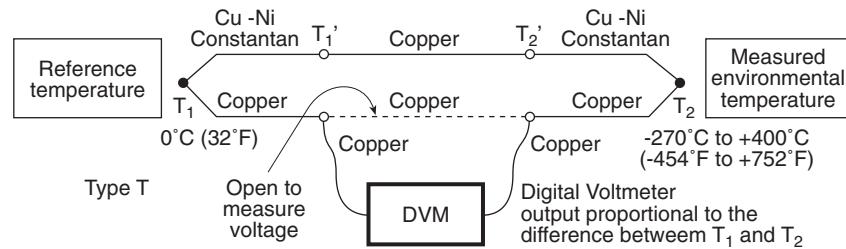

A basic thermocouple measurement system requires two sensors, one for the environment under measurement and the other, a reference junction, normally held to 0°C (32°F). Type-T is one of the dozen or more common thermocouples frequently used in general-purpose temperature measuring applications. It is made of copper and constantan metals and typically operates from -160° to 400°C (-328° to 662°F).

**Figure 2: Common Thermocouple Types**

Common Thermocouple Types								
Type	Metal		Standard color code	$\Omega/\text{double foot}$ 20 AWG	Seebeck coefficient $S(\mu\text{V}/^\circ\text{C}) @ T(^\circ\text{C})$	$^\circ\text{C}$ standard wire error	NBS specified materials range* ( $^\circ\text{C}$ )	
+	-	+	-					
B	Platinum-6% Rhodium	Platinum-30% Rhodium	Violet	0.2	6	600	4.4 to 8.6	0 to 1820**
E	Nickel-10% Chromium	Constantan	Red	0.71	58.5	0	1.7 to 4.4	-270 to 1000
J	Iron	Constantan	White	0.36	50.2	0	1.1 to 2.9	-210 to 760
K	Nickel-10% Chromium	Nickel	Yellow	0.59	39.4	0	1.1 to 2.9	-270 to 1372
N (AWG 14)	Nicrosil	Nisil	—	—	39	600	—	0 to 1300
N (AWG 28)	Nicrosil	Nisil	—	—	26.2	0	—	-270 to 400
R	Platinum-13% Rhodium	Platinum	—	0.19	11.5	600	1.4 to 3.8	-50 to 1768
S	Platinum-10% Rhodium	Platinum	—	0.19	10.3	600	1.4 to 3.8	-50 to 1768
T	Copper	Constantan	Blue	0.30	38	0	0.8 to 2.9	-270 to 400
W-Re	Tungsten-5% Rhenium	Tungsten-26% Rhenium	—	—	19.5	600	—	0 to 2320

\* Material range is for 8 AWG wire; decreases with decreasing wire size

\*\* Type B double-valued below 42°C – curve fit specified only above 130°C

NIST's (*National Institute of Standards and Technology*) thermocouple tables list the emf output of a thermocouple based on a corresponding reference junction held at 0°C.

In principle, a TC can be made from any two dissimilar metals such as nickel and iron. In practice, however, only a few TC types have become standard because their temperature coefficients are highly repeatable, they are rugged, and they generate relatively large output voltages. The most common thermocouple types are called J, K, T, and E, followed by N28, N14, S, R, and B. See the table in Figure 2. The junction temperature could be inferred from the Seebeck voltage by consulting standard tables. However, this voltage cannot be used directly because the thermocouple wire connection to the copper terminal at the measurement device itself constitutes a thermocouple junction (unless the TC lead is also copper) and generates another emf that must be compensated.


### Cold Junction Compensation

The classical method used to compensate the emf at the instrument terminals is shown in Figure 3. Here, a cold-reference junction thermocouple J2 is immersed in an actual ice-water bath and connects in series with the measuring thermocouple J1. The ice and water combination holds the temperature bath to a constant and accurate 0°C (32°F). NIST's thermocouple emf tables list the emf output of a thermocouple based on a corresponding reference thermocouple junction held at 0°C.

Figure 3 also depicts an example of a single thermocouple J1 with its constantan wire connected to a copper lead wire (J2) and immersed in the reference ice-water bath. The constantan/copper thermocouple junction J<sub>2</sub> in the ice bath still comprises a thermocouple and contributes a small emf that subtracts from the emf generated by thermocouple J<sub>1</sub>. Like the previous example, the voltage measured at the instrument or data acquisition system input terminals correspond accurately to the NIST tables.

In this example, both copper leads connect to the isothermal block on the instrument. These leads do not require compensation because they are made of the same material and are held at the same

**Figure 3: Alternate Thermocouple Ice Bath**

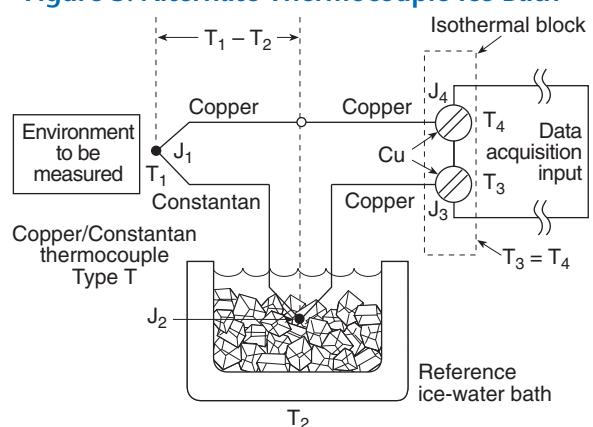

Whether J2 is a purchased thermocouple or not, the junction formed by the constantan and copper lead wires at J2 must be placed in the ice bath for temperature compensation.


temperature. Hence, the voltage reading comes entirely from the NIST-adjusted constantan/copper thermocouple wire.

### Software Compensation


Ice baths and multiple reference junctions in large test fixtures are nuisances to set up and maintain, and fortunately they all can be eliminated. The ice bath can be ignored when the temperature of the lead wires and the reference junction points (isothermal terminal block at the instrument) are the same. The emf correction needed at the terminals can be referenced and compensated to the NIST standards through computer software.

When ice baths are eliminated, cold junction compensation (CJC) is still necessary in order to obtain accurate thermocouple measurements. The software has to read the isothermal block

**Figure 4: Eliminating the Ice Bath**

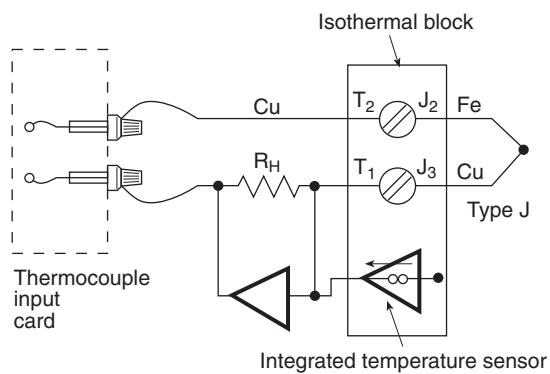

**Figure 5: Hardware Ice-Bath Replacement**

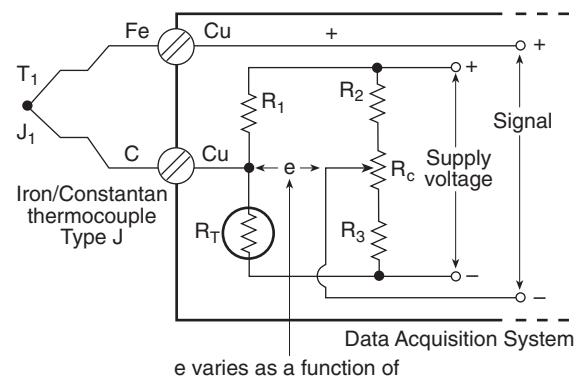

A thermistor sensor placed near the lead wire connections is an alternative method of replacing the ice bath. The measured temperature is the difference between the thermocouple temperature and the reference thermistor temperature.

temperature. One common technique uses a thermistor, mounted close to the isothermal terminal block that connects to the external thermocouple leads. No temperature gradients are allowed in the region containing the thermistor and terminals. See Figure 4. The type of thermocouple employed is preprogrammed for its respective channel, and the dynamic input data for the software includes the isothermal block temperature and the measured environmental temperature. The software uses the isothermal block temperature and type of thermocouple to look up the value of the measured temperature corresponding to its voltage in a table, or it calculates the temperature with a polynomial equation. The latter method allows numerous channels of thermocouples of various types to be connected simultaneously while the computer handles all the conversions automatically.

#### Hardware Compensation

Although a polynomial approach is faster than a look-up table, a hardware method is even faster, because the correct voltage is immediately available to be scanned. One method uses a battery in the circuit to null the offset voltage from the reference junction so the net effect equals a 0°C junction. A more practical approach is an “electronic ice point reference,” which generates a compensating voltage as a function of the temperature sensing circuit powered by a battery or similar voltage source. See Figure 5. The voltage then corresponds to an equivalent reference junction at 0°C.

#### Type Mixing

Thermocouple test systems often measure tens to hundreds of points simultaneously. In order to conveniently handle such large numbers of channels without the complication of separate, unique compensation TCs for each, thermocouple-scanning modules come with multiple input channels and can accept any of the various types of thermocouples on any channel, simultaneously. They contain special copper-based input terminal blocks with numerous cold junction compensation sensors to ensure accurate readings, regardless of

A number of electronic circuits or modules can replace the ice-bath. The temperature-sensitive resistor changes the calibrated value of voltage  $e$  in proportion to the amount of temperature compensation required.

the sensor type used. Moreover, the module contains a built-in automatic zeroing channel as well as the cold-junction compensation channel. Although measurement speed is relatively slower than most other types of scanning modules, the readings are captured in ms, they contain less noise, and they are more accurate and stable. For example, one TC channel can be measured in 3 ms, 14 channels in 16 ms, and 56 channels in 61 ms. Typical measurement accuracies are better than 0.7°C, with channel-to-channel variation typically less than 0.5°C. See Figure 6.


#### Linearization

After setting up the equivalent ice point reference emf in either hardware or software, the measured thermocouple voltage must be converted to a temperature reading. Thermocouple output voltage is proportional to the temperature of the TC junction, but it is not perfectly linear over a very wide range.

The standard method for obtaining high conversion accuracy for any temperature uses the value of the measured thermocouple voltage plugged into a characteristic equation for that particular type thermocouple. The equation is a polynomial with an order of six to ten. The computer automatically handles the calculation, but high-order polynomials take considerable time to process. In order to accelerate the calculation, the thermocouple characteristic curve is divided into several segments. Each segment is then approximated by a lower order polynomial.

Analog circuits are employed occasionally to linearize the curves, but when the polynomial method is not used, the thermocouple output voltage frequently connects to the input of an analog to digital converter (ADC) where the correct voltage to temperature match is obtained from a table stored in the computer’s memory. For example, one data acquisition system TC card includes a software driver that contains a temperature conversion library that changes raw binary TC channels and CJC information into temperature readings. Some software packages supply CJC information and automatically linearize the thermocouples connected to the system.

**Figure 6: Hardware Ice-Bath Replacement**

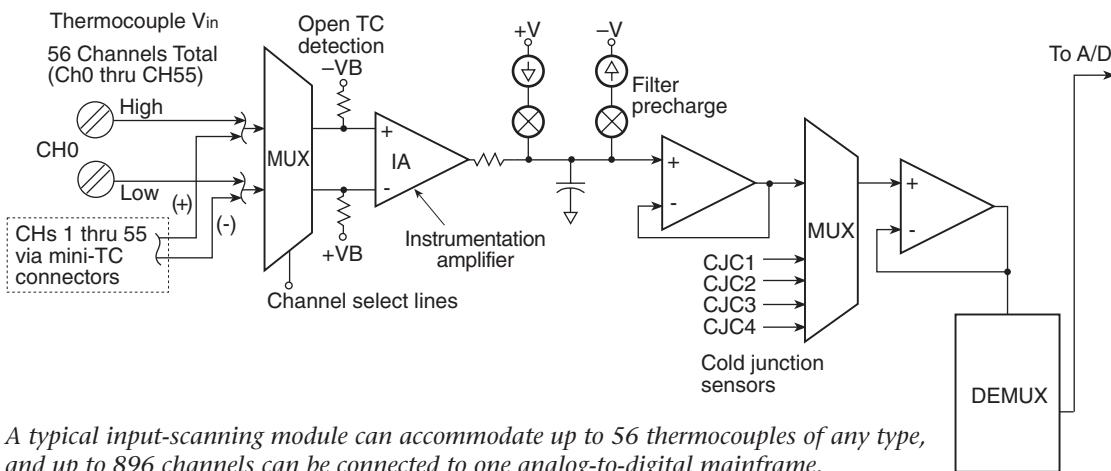

## Thermocouple Measurement Pitfalls

### Noisy Environments

Because thermocouples generate a relatively small voltage, noise is always an issue. (Also see TechTip 60402.) The most common source of noise is the utility power lines (50 or 60 Hz). Thermocouple bandwidth is lower than 50 Hz, so a simple filter in each channel can reduce the interfering ac line noise. Common filters include resistors and capacitors and active filters built around op amps. Although a passive RC filter is inexpensive and works well for analog circuits, it's not recommended for a multiplexed front end because the multiplexer's load can change the filter's characteristics. On the other hand, an active filter composed of an op amp and a few passive components works well, but it's more expensive and complex. Moreover, each channel must be calibrated to compensate for gain and offset errors. See Figure 7.


### Additional Concerns

#### Thermocouple Assembly

Thermocouples are twisted pairs of dissimilar wires and soldered or welded together at the junction. When not assembled properly, they can produce a variety of errors. For example, wires should not be twisted together to form a junction; they should be soldered or welded. But solder is sufficient only at relatively low temperatures, usually less than 200°C. And although soldering also introduces a third metal, such as a lead/tin alloy, it will not likely introduce errors if both sides of the junction are at the same temperature. Welding the junction is preferred, but it must be done without changing the wires' characteristics. Commercially manufactured thermocouple junctions are typically joined with capacitive discharge welders that ensure uniformity and prevent contamination.


Thermocouples can become un-calibrated and indicate the wrong temperature when the physical makeup of the wire is altered. Then it cannot meet the NIST standards. The change can come from a variety of sources, including exposure to temperature extremes, cold working the metal, stress placed on the cable when installed, vibration, or temperature gradients.

**Figure 7a: Passive Filters**

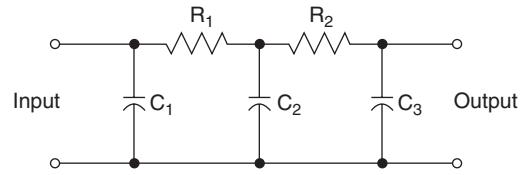

Passive filters come in a variety of configurations to suit the application. They are built in single or multiple sections to provide increasingly steeper slopes for faster roll-off.


**Figure 7b: Active Filters**

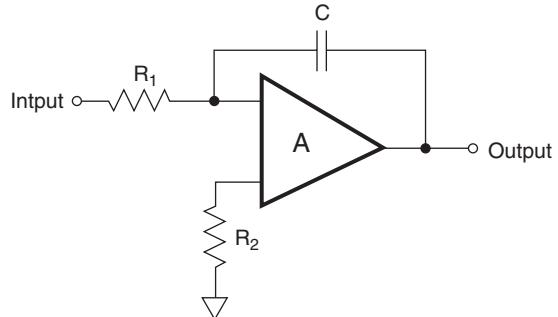

An active filter easily eliminates the most common sources of electrical noise that competes with the thermocouple signal—such as the interference from 50/60 Hz supply lines.

The output of the thermocouple also can change when its insulation resistance decreases as the temperature increases. The change is exponential and can produce a leakage resistance so low that it bypasses an open-thermocouple wire detector circuit. In high-temperature applications using thin thermocouple wire, the insulation can degrade to the point of forming a virtual junction as illustrated in Figure 8. The data acquisition system will then measure the output voltage of the virtual junction at T<sub>1</sub> instead of the true junction at T<sub>2</sub>.

**Figure 8: Virtual Junction**

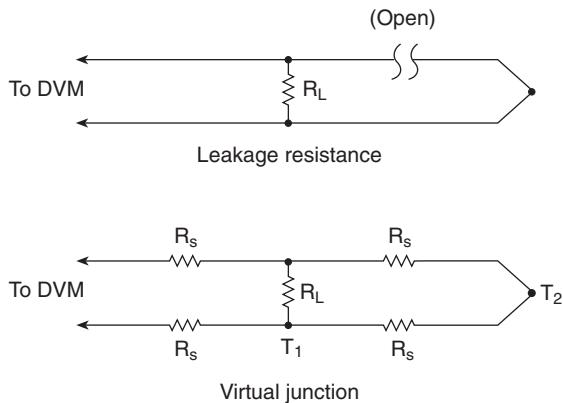

A short circuit or an insulation failure between the leads of a thermocouple can form an unwanted, inadvertent thermocouple junction called a virtual junction.

In addition, high temperatures can release impurities and chemicals within the thermocouple wire insulation that diffuse into the thermocouple metal and change its characteristics. Then, the temperature vs. voltage relationship deviates from the published values. Choose protective insulation intended for high-temperature operation to minimize these problems.

#### Isolation

Thermocouple isolation reduces noise and errors typically introduced by ground loops. This is especially troublesome where numerous thermocouples with long leads fasten directly between an engine block (or another large metal object) and the thermocouple-measurement instrument. They may reference different grounds, and without isolation, the ground loop can introduce relatively large errors in the readings.

#### Auto-Zero Correction


Subtracting the output of a shorted channel from the measurement channel's readings can minimize the effects of time and temperature drift on the system's analog circuitry. Although extremely small, this drift can become a significant part of the low-level voltage supplied by a thermocouple.

One effective method of subtracting the offset due to drift is done in two steps. First, the internal channel sequencer switches to a reference node and stores the offset error voltage on a capacitor. Next, as the thermocouple channel switches onto the analog path, the stored error voltage is applied to the offset correction input of a differential amplifier and automatically nulls out the offset. See Figure 9.

#### Open Thermocouple Detection


Detecting open thermocouples easily and quickly is especially critical in systems with numerous channels. Thermocouples tend to break or increase in resistance when exposed to vibration, poor handling, and long service time. A simple open-thermocouple detection circuit comprises a small capacitor placed across the thermocouple leads and driven with a low-level current. The low impedance of the intact thermocouple

**Figure 9: Auto-Zero Correction**

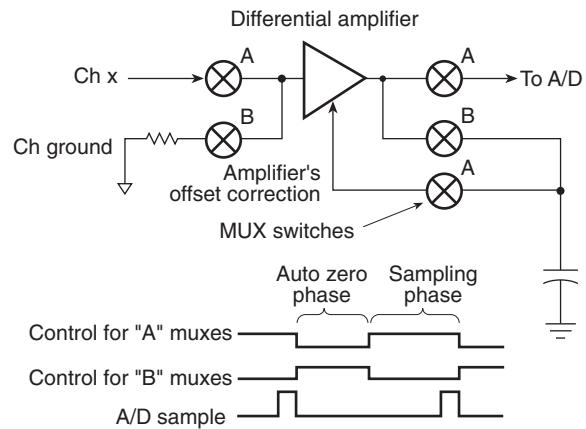

Auto-Zero Correction compensates for analog circuitry drift over time and temperature. Although small, the offset could approach the magnitude of the thermocouple signal.

**Figure 10: Open Thermocouple Detector**

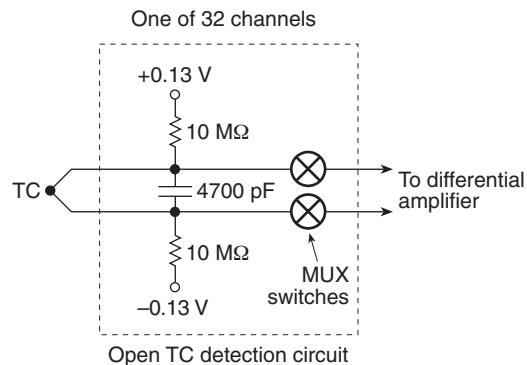

The thermocouple provides a short-circuit path for dc around the capacitor, preventing it from charging through the resistors. When the thermocouple opens, due to rough handling or vibration, the capacitor charges and drives the input amplifier to the power supply rails, signaling a failure.

presents a virtual short circuit across the capacitor so it cannot charge. But when a thermocouple opens or significantly changes resistance, the capacitor charges and drives the input to one of the voltage rails, which positively indicates a defective thermocouple. See Figure 10.

#### Galvanic Action

Some thermocouple insulating materials contain dyes that form an electrolyte in the presence of water. The electrolyte generates a galvanic voltage between the leads, which in turn, produces output signals hundreds of times greater than the net open-circuit voltage. Thus, good installation practice calls for shielding the thermocouple wires from high humidity and all liquids to avoid such problems.

## Thermal Shunting

An ideal thermocouple does not affect the temperature of the device being measured, but a real thermocouple comprises a mass that when added to the device under test can alter the temperature measurement. Thermocouple mass can be minimized with small diameter wires, but smaller wire is more susceptible to contamination, annealing, strain, and shunt impedance. One solution to help ease this problem is to use the small thermocouple wire at the junction but add special, heavier thermocouple extension wire to cover long distances. The material used in these extension wires has net open-circuit voltage coefficients similar to specific thermocouple types. Its series resistance is relatively low over long distances, and it can be pulled through conduit more easily than premium grade thermocouple wire. In addition to its practical size advantage, extension wire is less expensive than standard thermocouple wire, especially platinum.

Despite these advantages, extension wire generally operates over a much narrower temperature range and is more likely to receive mechanical stress. For these reasons, temperature gradients across the extension wire should be kept to a minimum to ensure accurate temperature measurements.

## Improving Wire Calibration Accuracy

Thermocouple wire is manufactured to NIST specifications. Often, these specifications can be more closely met when the wire is calibrated on site against a known temperature standard.

## PART B — RTD MEASUREMENTS

### Basics of Resistance Temperature Detectors

Platinum RTD resistances range from about  $10\ \Omega$  for a birdcage configuration to  $10k\ \Omega$  for a film type, but the most common is  $100\ \Omega$  at  $0^\circ\text{C}$ . Commercial platinum wire has a standard temperature coefficient, called alpha, of  $0.00385\ \Omega/\Omega/{^\circ\text{C}}$ , and chemically pure platinum has a coefficient of  $0.00392\ \Omega/\Omega/{^\circ\text{C}}$ .

A nominal  $100\text{-}\Omega$  platinum wire at  $0^\circ\text{C}$  will change resistance, either plus or minus, over a slope of  $0.385\ \Omega/{^\circ\text{C}}$ . For example, a  $10^\circ\text{C}$  rise in temperature will change the output of the sensor from  $100\ \Omega$  to  $103.85\ \Omega$ , and a  $10^\circ\text{C}$  fall in temperature will change the RTD resistance to  $96.15\ \Omega$ .

Because RTD sensor resistances and temperature coefficients are relatively small, lead wires with a total resistance as low as  $10\ \Omega$  and relatively high temperature coefficients can change the data acquisition system's calibration. The lead wire's resistance change over temperature can add to or subtract from the RTD sensor's output and produce appreciable errors in temperature measurement.

The resistance of the RTD (or any resistor) is determined by passing a measured current through it from a known voltage source. The resistance is then calculated using Ohms Law. To eliminate the measurement error contributed by lead wires, a second set of voltage sensing leads should be connected to the sensor's terminals and the opposite ends connected to corresponding sense terminals at the signal conditioner. This is called a four-wire RTD measurement. The sensor voltage is measured directly and eliminates the voltage drop in the current carrying leads.


## Measurement Approaches

### Configurations: 2, 3 and 4-wire

Five types of circuits are used for RTD measurements using two, three, and four lead wires: Two-wire with current source, four-wire with current source, three-wire with current source, four-wire with voltage source, and three-wire with voltage source.

Figure 11 shows a basic two-wire resistance measurement method. The RTD resistance is measured directly from the Ohmmeter. But this connection is rarely used since the lead wire resistance and temperature coefficient must be known. Often, both properties are not known, nor are they convenient to measure when setting up a test.


Figure 11: Two-Wire RTD

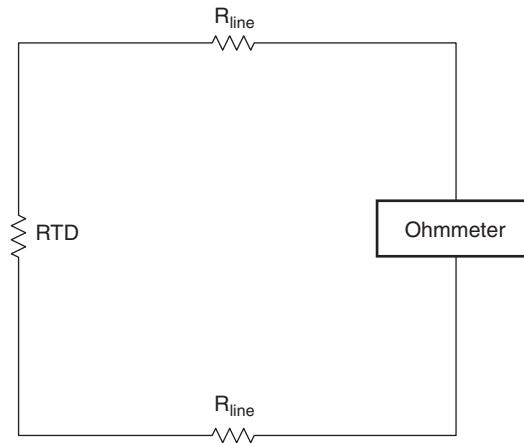

The simplest arrangement for an RTD measurement is a series circuit containing only two wires connected to an Ohmmeter.

Figure 12 shows a basic four-wire measurement method using a current source. The RTD resistance is  $V/I$ . This connection is more accurate than the two-wire method, but it requires a high stability current source and four lead wires. Because the high-impedance voltmeter does not draw appreciable current, the voltage across the RTD equals  $V_m$ .

Figure 12: Four-Wire RTD With Current Source

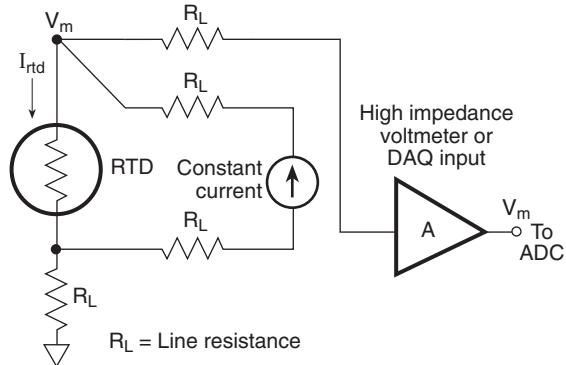

The four-wire RTD method with a current supply eliminates the lead wire resistance as a source of error.

### Equation 1: Four-Wire RTD With Current Source

$$R_{\text{RTD}} = \frac{V_m}{I_{\text{RTD}}}$$


Where:  $R_{\text{RTD}}$  = RTD resistance,  $\Omega$

$V_m$  = Voltmeter reading, V

$I_{\text{RTD}}$  = RTD current, A

Figure 13 shows a three-wire measurement technique using a current source. The symbols  $V_a$  and  $V_b$  represent two voltages measured by the high-impedance voltmeter in sequence through switches  $S_1$  and  $S_2$  (or a multiplexer). The RTD resistance is derived from Kirchhoff's voltage law and the solution of two simultaneous equations. (Illustrating the solution is beyond the scope of this TechTip.) The benefit of this connection over that shown in Figure 12 is one less lead wire. However, this connection assumes that the two current-carrying wires have the same resistance.
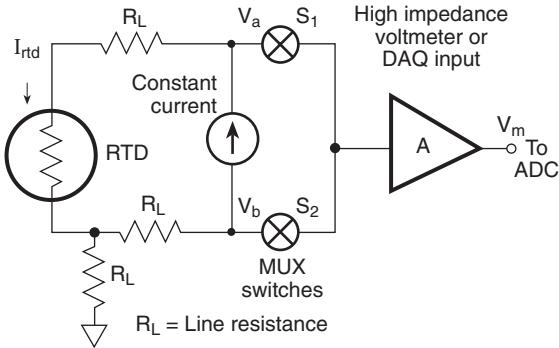
### Figure 13: Three-Wire RTD With Current Source




The three-wire RTD method with a current supply is similar to the four-wire method. It simply eliminates one additional wire.

### Equation 2: Three-Wire RTD With Current Source

$$R_{\text{RTD}} = \frac{V_a - V_b}{I_{\text{RTD}}}$$

Figure 14 shows a four-wire measurement system using a voltage source. The RTD resistance also is derived from Kirchhoff's voltage law and four simultaneous equations based on the four voltages,  $V_a$  through  $V_d$ . The voltage source in this circuit can vary somewhat as long as the sense resistor remains stable.
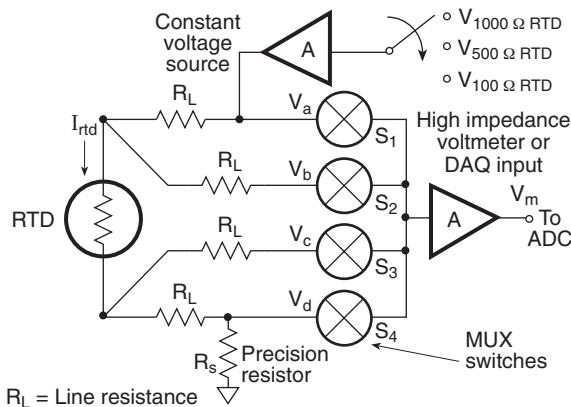
### Figure 14: Four-Wire RTD With Voltage Source




The four-wire RTD circuit with a voltage source is more complex than the four-wire with current source, but the voltage is allowed to vary somewhat provided the sense resistor is stable.

### Equation 3: Four-Wire RTD With Voltage Source

$$R_{\text{RTD}} = \frac{R_s (V_b - V_c)}{V_d}$$

Figure 15 shows a three-wire measurement technique using a voltage source. The RTD resistance is derived from Kirchhoff's voltage law and three simultaneous equations. The voltage source can vary as long as the sense resistor remains stable, and the circuit is accurate as long as the resistances of the two current-carrying wires are the same.
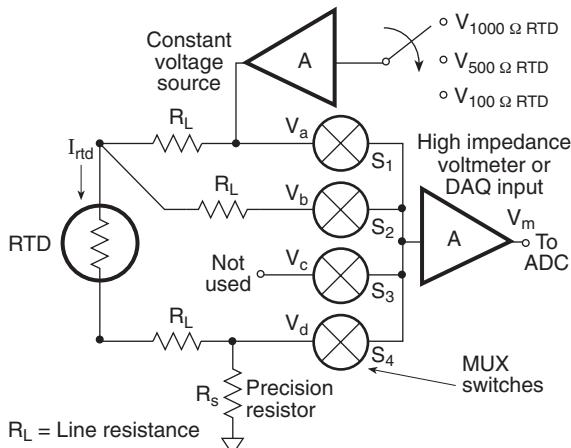
### Figure 15: Three-Wire RTD With Voltage Source



This is a variation of the four-wire circuit with voltage source and a stable sense resistor.

### Equation 4: Three-Wire RTD With Voltage Source

$$R_{\text{RTD}} = \frac{R_s (2V_b - V_a - V_d)}{V_d}$$


The RTD output is more linear than the thermocouple, but its range is smaller.

The Callendar-Van Dusen equation,

$$R_T = R_0 + R_0 \alpha \left[ T - \delta \left( \frac{T}{100} - 1 \right) \left( \frac{T}{100} \right) - \beta \left( \frac{T}{100} - 1 \right) \left( \frac{T^3}{100} \right) \right]$$

is often used to calculate the RTD resistance, but it can be cumbersome to use. An alternative method involves measuring RTD resistances at four temperatures and solving a 20<sup>th</sup> order polynomial equation with these values. It provides more precise data than does the alpha, sigma, and beta coefficients in the Callendar-Van Dusen equation. The plot of the polynomial equation in Figure 16 shows the RTD to be more linear than the thermocouple when used below 800°C, the maximum temperature for RTDs.

**Figure 16: Type S Thermocouple vs. Platinum RTD**

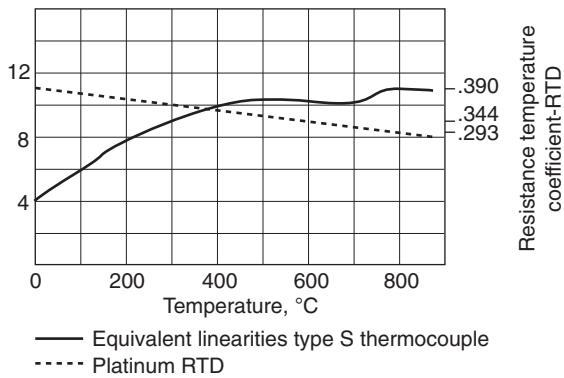

Platinum is the material of choice for RTDs and thermocouples because it is stable and resists corrosion. Here, the RTD is shown to be more linear under temperatures of 800 C than the thermocouple.

### Self-Heating

Another source of error in RTD measurements is resistive heating. The current, I, passing through the RTD sensor, R, dissipates power, P, where  $P = I^2R$ . For example, 1 mA through a 100-Ω RTD generates 100 µW. This may seem insignificant, but it can raise the temperature of some RTDs a significant fraction of a degree. A typical RTD can change 1°C/mW by self-heating. When selecting smaller RTDs for faster response times, consider that they also can have larger self-heating errors.

A typical value for self-heating error is 1°C/mW in free air. An RTD immersed in a thermally conductive medium distributes this heat to the medium and the resulting error is smaller. The


same RTD rises 0.1°C/mW in air flowing at 1 m/s. Using the minimum excitation current that provides the desired resolution, and using the largest physically practical RTD will help reduce self-heating errors.

### Scanning Inputs

Since lower currents generate less heat, currents between 100 and 500 µA are typically used. This lowers the power dissipation to 10 to 25 µW, which most applications can tolerate. Further reducing the current lowers accuracy because they become more susceptible to noise and are more difficult to measure. But switching the current on only when the measurement is made can reduce the RTD's heat to below 10 µW. In a multichannel system, for example, the excitation current can be multiplexed, much like the analog inputs. In a 16-channel system, the current will only excite each RTD 1/16<sup>th</sup> of the time, reducing the power delivered to each RTD from 100% to only 6%.

Two practical methods for scanning an RTD include constant current and ratiometric. An example of a constant current circuit is shown in Figure 17. It's an RTD scanning module, which switches a single 500 µA constant current source among 16 channels. A series of front-end multiplexers direct the current to each channel sequentially while the measurement is being taken. Both three and four-wire connections are supported to accommodate both types of RTDs. By applying current to one RTD at a time, errors due to resistive heating become negligible. Advantages of the constant current method include simple circuits and noise immunity. But the disadvantage is the high cost of buying or building an extremely stable constant current source.


**Figure 17: Constant-Current Scanning Module**

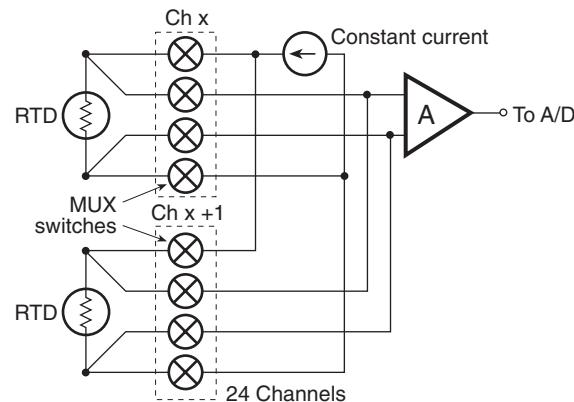

The constant-current source is sequentially switched among the various RTD sensors to keep them cooler over the measurement interval and prevent resistive-heating errors.

By contrast, the ratiometric method uses a constant voltage source to provide a current,  $I_s$ , through the RTD and a resistor,  $R_d$ . Four voltage readings are taken for each RTD channel,  $V_a$ ,  $V_b$ ,  $V_c$ , and  $V_d$ . Refer to Figure 18.

**Figure 18: Ratiometric Four-Wire RTD**

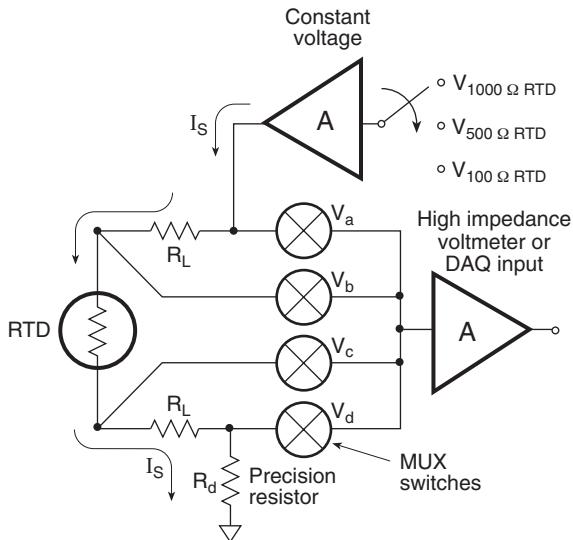

Four voltage readings are taken for each RTD channel. The precision resistor measures  $I_s$ , the RTD current;  $V_b$  and  $V_c$  measure the RTD voltage; and the RTD resistance equals  $(V_b - V_c)/I_s$ .

The current, voltage, and resistance of the RTD is:

**Equation 5: Four-Wire RTD Ratiometric Measurement**

$$I_s = \frac{V_d}{R_d}$$

$$V_{\text{RTD}} = V_b - V_c$$

$$R_{\text{RTD}} = \frac{V_{\text{RTD}}}{I_s}$$


For the three-wire connection shown in Figure 19, the voltage,  $V_a - V_c$ , includes the voltage drop across only one lead. Because the two extension wires to the transducer are made of the same metal, assume that the drop in the first wire is equal to the drop in the second wire. Therefore, the voltage across the RTD and its resistance is:

**Equation 6: Three-Wire RTD Ratiometric Measurement**

$$V_{\text{RTD}} = V_a - 2(V_a - V_b) - V_d$$

$$R_{\text{RTD}} = R_d \left( \frac{V_{\text{RTD}}}{V_d} \right)$$

**Figure 19: Ratiometric Three-Wire RTD with Switched Voltage**

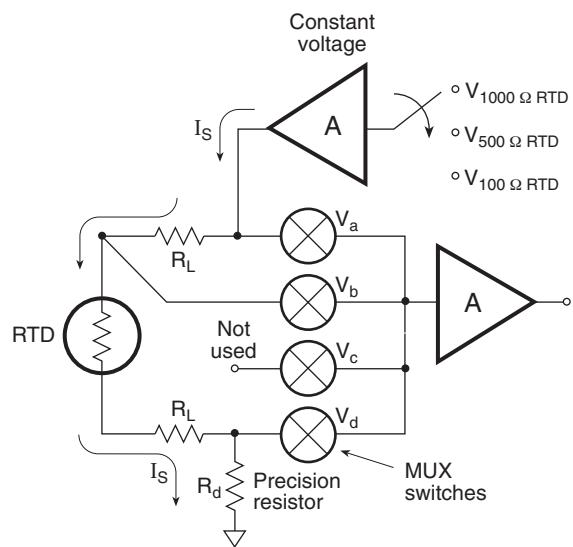

The three-wire ratiometric circuit assumes that both sense-wire resistances in the four-wire circuit are the same. The equation for calculating RTD resistance simply accounts for it with a factor of two.

#### Practical Precautions

RTDs require the same precautions that apply to thermocouples, including using shields and twisted-pair wire, proper sheathing, avoiding stress and steep gradients, and using large diameter extension wire. In addition, the RTD is more fragile than the thermocouple and needs to be protected during use. Also, thermal shunting is a bigger concern for RTDs than for thermocouples because the mass of the RTD is generally much larger. See Figure 20.

**Figure 20: RTD Resistance Comparison**

RTD Resistance Comparison: Small Resistance vs. Large Resistance		
	Small RTD	Large RTD
Response time	Fast	Slow
Thermal shunting	Low	Poor
Self-heating error	High	Low

Although smaller RTDs respond faster to temperature changes, they are more susceptible to inaccuracy from self-heating.

## PART C — THERMISTOR MEASUREMENTS

### Basics of Thermistors

Thermistors are generally composed of semiconductor materials or oxides of common elements such as cobalt, copper, iron, manganese, magnesium, nickel, and others. They typically come with 3 to 6-in. leads, encapsulated, and color-coded. They are available in a range of accuracies from  $\pm 15^\circ\text{C}$  to  $\pm 1^\circ\text{C}$ , with a nominal resistance ranging from  $2,000 \Omega$  to  $10,000 \Omega$  at  $25^\circ\text{C}$ . A value of  $2252 \Omega$  is common and can be used with most instruments. A plot of the temperature vs. resistance characteristic curves is usually provided with the device to determine the temperature from a known resistance. However, the devices are highly non-linear and the following equation may be used to calculate the temperature:

### Equation 7: Thermistor Temperature

$$\frac{1}{T} = A + B(\log_e R) + C(\log_e R)^3$$


Where:  $T$  = temperature,  $^\circ\text{K}$

$A$ ,  $B$ , and  $C$  = fitting constants

$R$  = resistance,  $\Omega$

The constants  $A$ ,  $B$ , and  $C$  are calculated from three simultaneous equations with known data sets: Insert  $R_1$  and  $T_1$ ;  $R_2$  and  $T_2$ ;  $R_3$  and  $T_3$ , then solve for  $A$ ,  $B$ , and  $C$ . Interpolation yields a solution accurate to  $+\/- 0.01^\circ\text{C}$  or better. (Illustrating the procedure is beyond the scope of this TechTip.)

**Figure 21 (6.22): Linearize Thermistor Output Voltage**

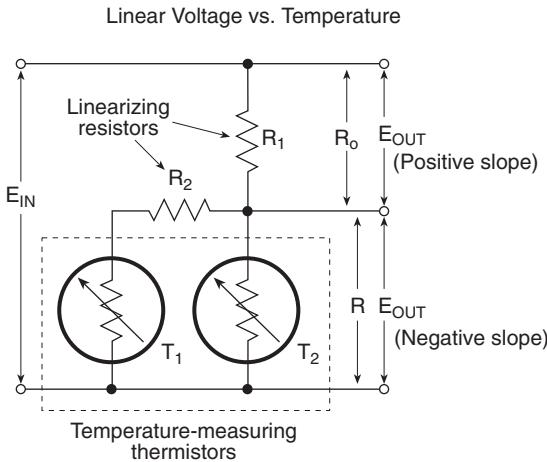

The compensating resistors in series with the thermistors improve linearity near the center of the thermistor's S-shaped characteristic curve. This is where the sensitivity is the greatest, and its operating temperatures can be extended to cover a wider range.

### Linearization

Some thermistor manufacturers supply devices that provide a near-linear output. They use multiple thermistors (positive and negative coefficients) or a combination of thermistors and metal film resistors in a single package. When connected in certain networks, they produce a linearly varying voltage or

resistance proportional to temperature. A widely used equation for the voltage divider shown in Figure 21 is:

### Equation 8: Thermistor Voltage Divider

$$E_{\text{out}} = E_{\text{in}} \left( \frac{R}{R + R_0} \right)$$

Where:  $E_{\text{out}}$  is the voltage drop across  $R$

If  $R$  is a thermistor, and the output voltage is plotted against the temperature, the curve resembles an S-shape with a fairly straight center portion. However, adding other resistors or thermistors to  $R$  linearizes the center portion of the curve over a wider temperature range. See Figure 22. The linear section follows the equation of a straight line,  $Y = mX + b$ .

For the voltage mode:

### Equation 9: Thermistor Voltage Mode

$$E_{\text{out}} = \pm MT + b$$

Where:  $T$  = temperature in  $^\circ\text{C}$  or  $^\circ\text{F}$

$b$  = value of  $E_{\text{out}}$  when  $T = 0$

$M$  = slope, volts per degree  $T$  in  $^\circ\text{C}$  or  $^\circ\text{F}$ ,  $\text{V}/^\circ\text{C}$  or  $\text{V}/^\circ\text{F}$

For the resistance mode, see Figure 22:

### Equation 10: Thermistor Resistance Mode

$$R_t = MT + b$$


Where:  $T$  = temperature in  $^\circ\text{C}$  or  $^\circ\text{F}$

$b$  = value of the total network resistance

$R_t$  in  $\Omega$  when  $T = 0$

$M$  = slope,  $\Omega$  per degree  $T$  in  $^\circ\text{C}$  or  $^\circ\text{F}$ ,  $\Omega/^\circ\text{C}$  or  $\Omega/^\circ\text{F}$

**Figure 22: Linearize Thermistor Output Resistance**

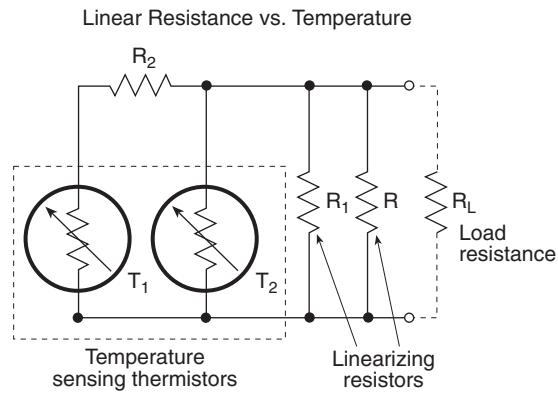

Compensating resistors in the network linearize the resistance change vs. temperature in the same manner as they do for the voltage mode.

Although a lot of research has gone into developing linear thermistors, most modern data acquisition system controllers and software handle the linearization, which makes hardware linearization methods virtually obsolete.

#### **Stability**

Thermistors are inherently and reasonably stable devices, not normally subject to large changes in nominal resistance with aging, nor with exposure to strong radiation fields. However, prolonged operation over 90° C can change the tolerance of thermistors, particularly those with values less than 2,000 Ω. They are smaller and more fragile than thermocouples and RTDs, so they cannot tolerate much mishandling.

#### **Time Constant**

The time required for a thermistor to reach 63% of its final resistance value after being thrust into a new temperature environment is called its time constant. The time constant for an unprotected thermistor placed in a liquid bath may range from 1 to 2.5 s. The same device exposed to an air environment might require 10 s, while an insulated unit could require up to 25 s. Seven time constants is a universally accepted value to consider that the device has reached its plateau or about 99% of its final value. Therefore a device in the liquid bath might take as long as 7 s to stabilize, while the same device in air could take 125 s or more than two minutes.

#### **Dissipation Constant & Operating Temperature**

The power required to raise the temperature of a thermistor 1° C above the ambient is called the dissipation factor. It is typically in the mW range for most devices. The maximum operating temperature for a thermistor is about 150° C.

#### **Tolerance curves**

Manufacturers have not standardized on thermistor characteristic curves to the extent they have for thermocouples and RTDs. Thermistors are well suited to measuring temperature set points, and each thermistor brand comes with its unique curve which is often used to design on/off control circuits.

## **PROCEDURE**

The following product tables list the IOtech equipment most suitable for measuring temperature. Some of the instruments contain built-in signal conditioners for handling thermocouples, RTDs, and thermistors. Other instruments are more general purpose and require WBK™ or DBK™ type plug-in modules to provide the proper signal conditioning.

The tables are intended to allow users to select the most appropriate data acquisition system for the job at the most reasonable cost. For example, the DaqTemp™ and Personal Daq™ instruments are the most economical and have built-in signal conditioning, but they cannot be used to measure low-level voltage signals. They are limited to temperature measurements. On the other hand, the LogBook™ can measure almost any variable, provided it has the appropriate signal-conditioning module. Although this configuration is more expensive, it may be most appropriate for users who have a requirement to measure a mix of many more variables and more channels.

Consult the instruction manual for each product when connecting the various temperature sensors. The manuals contain the details necessary to ensure a robust measurement system. They are available on IOtech's Web site for viewing whether you have the product in hand or are considering purchasing one. Visit our Web site at [www.iotech.com](http://www.iotech.com).

## **Contact Information**

**IOtech, Inc.**  
25971 Cannon Road  
Cleveland, Ohio 44146  
**Phone:** 1-440-439-4091  
**Fax:** 1-440-439-4093  
**Email:** [sales@iotech.com](mailto:sales@iotech.com)

**TABLE 1****IOtech Hardware for Temperature Measurements**

Product	Number of Possible Channels	Sensor	Signal Conditioner Options	PC Interface	Power Source	Software	Excel Link
<a href="#">DaqTemp</a>	7/14	TC	Built-in	PCI	PC	DaqView* DASYLab LabVIEW	Optional
<a href="#">Personal Daq/50</a>	10 to 60	TC	Built-in	USB	USB AC DC	Personal-DaqView* DASYLab LabVIEW	Optional
<a href="#">Personal Daq/3000</a>	16 to 32	TC	Built-in	USB	USB AC DC	DaqVIEW* DASYLab LabVIEW MATLAB	Optional
<a href="#">DaqScan</a>	896	TC	DBK42 DBK48 DBK90 DBK207/CJC DBK9	Ethernet	AC	DaqView* IVI Drivers DASYLab LabVIEW MATLAB	Optional
<a href="#">TempScan</a>	32 to 992	TC	TempTC/32B	IEEE.488, Serial	AC	ChartView* LabVIEW	Yes
<a href="#">MultiScan</a>	24 to 744	TC	MTC/24	IEEE.488, Serial	AC	ChartView* LabVIEW	Yes
<a href="#">ChartScan</a>	16 to 128	TC	CSN14/TC/P	IEEE.488, Serial Ethernet	AC	ChartView* LabVIEW	Yes
<a href="#">DaqBook</a>	7 to 856	TC	DBK42 DBK48 DBK81 DBK82 DBK83 DBK84 DBK90 DBK100 DBK9	Ethernet	AC, DC	DaqView* DASYLab LabVIEW MATLAB	Optional
<a href="#">DaqLab</a>	896	TC	DBK42 DBK48 DBK90 DBK207/CJC DBK9	Ethernet	AC	DaqView* DASYLab LabVIEW MATLAB	Optional
<a href="#">DaqBoard/3000USB Series</a>	4	TC	Built-in	USB	From PC	DaqView* DASYLab LabVIEW MATLAB	N/A
<a href="#">DaqBoard/3000</a>	24	TC	PDQ30	PCI	From PC	DaqView* DASYLab LabVIEW MATLAB	Optional

\* Supplied with product.

**TABLE 1 (continued)****IOtech Hardware for Temperature Measurements**

Product	Number of Possible Channels	Sensor	Signal Conditioner Options	PC Interface	Power Source	Software	Excel Link
<a href="#"><u>LogBook</u></a>	14 to 224	TC	DBK42 DBK81 DBK82 DBK83 DBK84	RS-232 Parallel	AC DC	LogView*	N/A
	8 to 128	RTD	DBK9				
<a href="#"><u>DaqBoard/2000</u></a>	7 to 14	TC	DBK81 DBK82 DBK83 DBK84 DBK207/CJC	PCI	From PC	DaqView* DASYLab LabVIEW MATLAB	Optional
	8	RTD	DBK9				

\* Supplied with product.

**Contact IOtech today for all your Temperature Measurement needs!**

**1-888-714-3272**

**[www.iotech.com](http://www.iotech.com)**

**[sales@iotech.com](mailto:sales@iotech.com)**

**TABLE 2****IOtech Hardware for Temperature Measurements**

Signal Conditioner Description	Number of Possible Channels	Sensor Type	Notes
<a href="#">DBK42</a> Isolated Signal Conditioning Module	16-slot	TC	Requires 5B-type modules (See catalog)
<a href="#">DBK48</a> Isolated Signal Conditioning Module	16-slot	TC/RTD	Requires 8B-type modules (See catalog)
<a href="#">DBK81</a>	7	TC/mV	
<a href="#">DBK82</a>	14	TC/mV	
<a href="#">DBK83</a>	14	TC/mV	
<a href="#">DBK84</a>	14	TC/mV	
<a href="#">DBK90</a>	56	TC	
<a href="#">DBK207CJC</a> (Cold Junction Compensation)	16	TC	5B Isolated Analog Signal Conditioning Module
<a href="#">PDQ30</a> Expansion Module	64	TC/mV	
<a href="#">TempTC/32B</a>	32	TC	
<a href="#">TempRTD/16B</a>	16	RTD	
<a href="#">MTC/24</a>	24	TC/mV	

**Contact IOtech today for all your Temperature Measurement needs!**

**1-888-714-3272**

**[www.iotech.com](http://www.iotech.com)**

**[sales@iotech.com](mailto:sales@iotech.com)**